

1.1.1. Testing a circuit

The screenshot displays a logic simulator window with a circuit diagram. On the left, there are two red switch components, each labeled with a '1' and a '0'. These switches are connected to the inputs of a central grey AND gate. The output of the AND gate is connected to two grey LED components on the right. A 'Palette' window is open on the right side of the screen, showing a grid of various logic components including gates, flip-flops, and other digital logic elements.

The diagram illustrates a logic circuit. On the left, there are two input variables, each represented by a red square with a white document icon and a '1' above a '0'. The top input is connected to the top input of a grey AND gate. The bottom input is connected to the bottom input of the same AND gate. The output of the AND gate is connected to two output variables, each represented by a grey square with a red document icon and a '1' above a '0'.

Table 1. LEDs working conditions.

Upper switch	Lower switch	LEDs
Off	Off	Off
Off	On	Off
On	Off	Off
On	On	On

The LEDs are working when both switches are on, the basic logic of an AND gate.

Table 2. The carry in the addition of two binary numbers.

Bit of #1 binary number	Bit of #2 binary number	Carry
0	0	0
0	1	0
1	0	0
1	1	1

So we see here the same logic: the carry is appearing only when the two summing digits are both equal to 1.

1.1.2. Changing a Circuit

Figure 3. The circuit with a NAND gate.

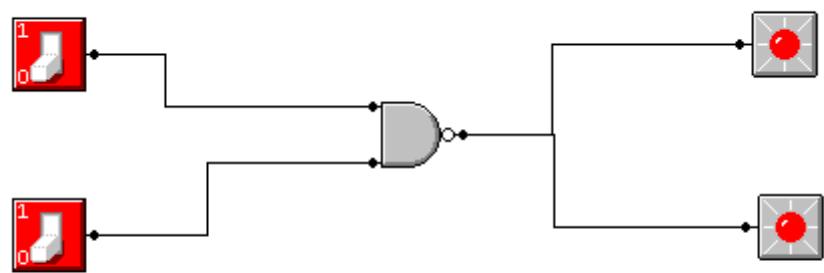


Table 3. The truth table for the NAND gate.

Upper switch	Lower switch	LEDs
Off	Off	On
Off	On	On
On	Off	On
On	On	Off

1.1.3 Making an adder

Figure 4. An adder circuit

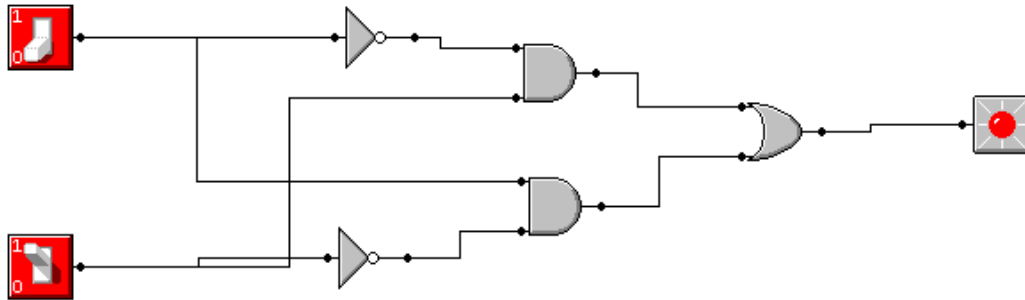


Table 4. The truth table for the adder circuit.


Upper switch	Lower switch	LEDs
Off	Off	Off
Off	On	On
On	Off	On
On	On	Off

Table 5. The truth table of a binary adder.

A	B	Z (LSB)
0	0	0
0	1	1
1	0	1
1	1	0

Result: They are the same.

Figure 5. The XOR circuit.

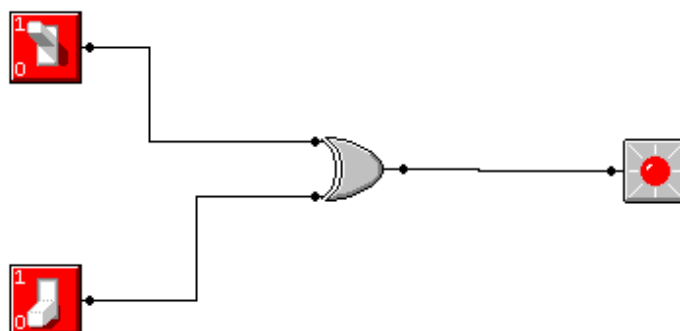

1.1.4 Adding with carry


Table 6. The circuit of adding with carry

Left upper switch	Left lower switch	Bottom switch	Upper LED	Lower LED
Off	Off	Off	Off	Off
Off	Off	On	Off	On
Off	On	Off	Off	On
Off	On	On	On	Off
On	Off	Off	Off	On
On	Off	On	On	Off
On	On	Off	On	Off
On	On	On	On	On

Figure 6. Truth table for a full adder

Full Adder
Truth
Table

Inputs			Outputs	
A	B	C _{in}	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

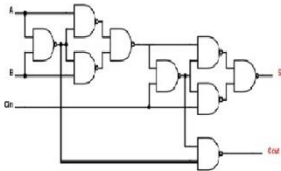

Result: Our circuit actually works as a full adder. It shows the MSB – Cout.

1.1.5. Adding two digits

Figure 7. The circuit that adds two digits.

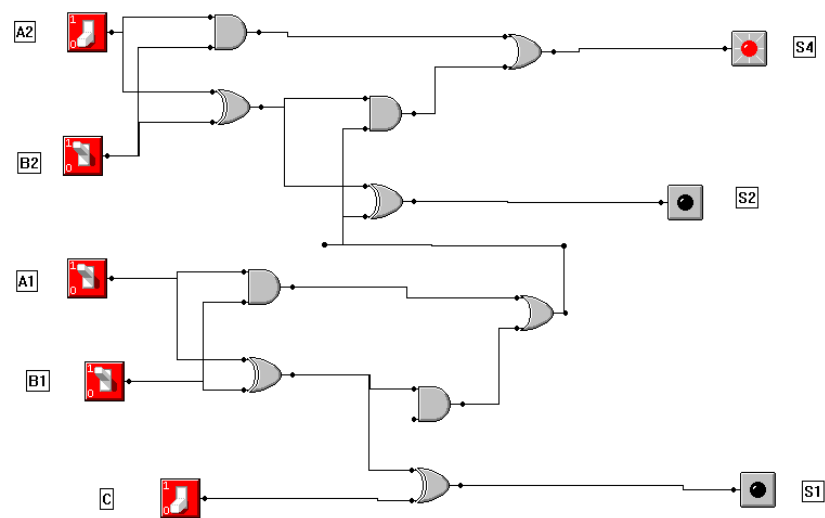


Table 7. Some values for adding two digits.

A_2	A_1	A	B_2	B_1	B	C	S_4	S_2	S_1
0	1	1	0	1	1	0	0	1	0
0	1	1	0	1	1	1	0	1	1
1	0	1	1	0	1	0	1	0	0
1	0	1	1	0	1	1	1	0	1

Answers:

a) Actually, this circuit can be perceived as one of the stages of an adder, where A2,A1 are the digits of one binary number, B2B1 of the other one, and C is the carry from the previous stage of the adder. Thus, S4 is the final carry which then can be used in another stage.

b) I think that the logic of the circuitry is the same, we just need to add some new switches and LEDs.

1.2 Electronic Dice

Part 1:

We fill out the table:

Figure 8. A table for an electronic dice.







		4 possible light patterns available				Count $Q_2Q_1Q_0$
		A	B	C	D	
Required pattern for each die roll		1				1 001_2
					1	2 010_2
		1			1	3 011_2
				1	1	4 100_2
		1		1	1	5 101_2
			1	1	1	6 110_2

Figure 9. K-maps


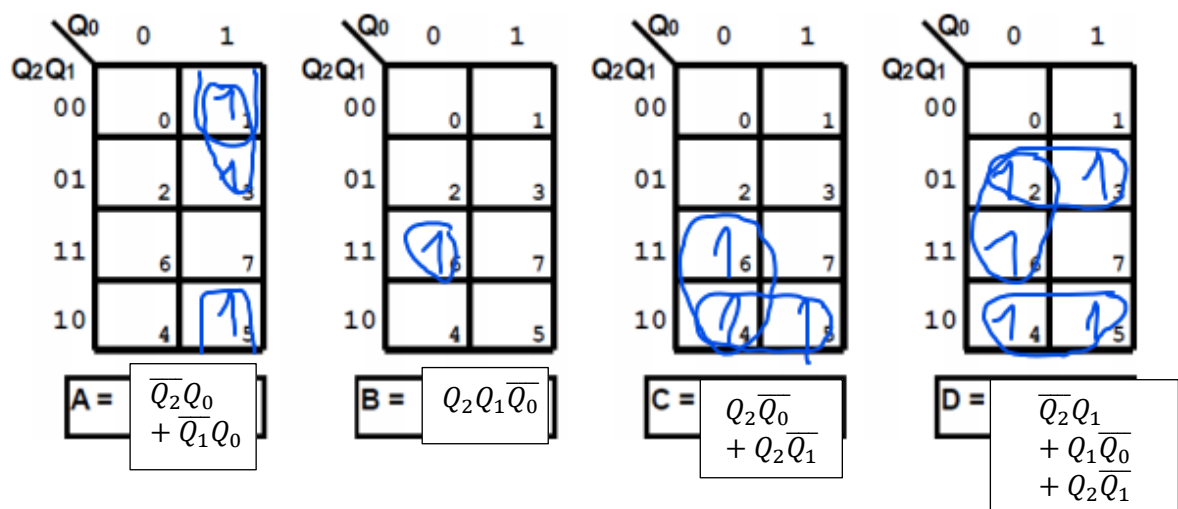


Figure 10. The circuit when 110_2 or 6 is activated.

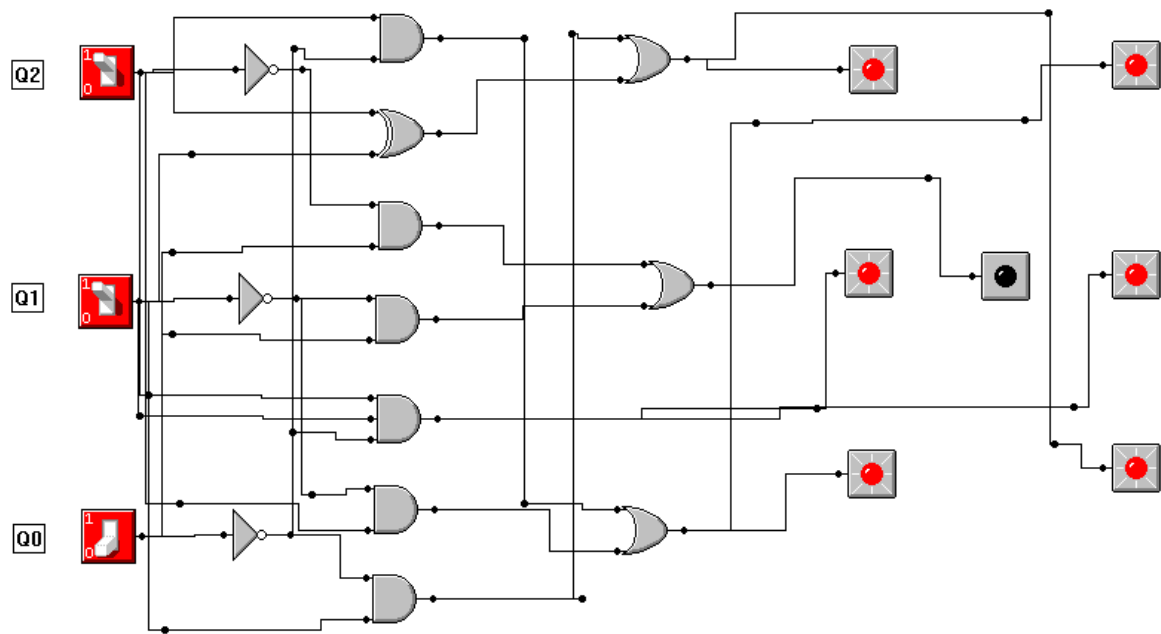

Part 2:


Figure 11. K-map for an asynchronous 4-bit counter.

		Q ₁ Q ₀			
		00	01	11	10
Q ₃ Q ₂	00	0 ₀	0 ₁	0 ₃	0 ₂
	01	0 ₄	0 ₅	X ₇	0 ₆
	11	X ₁₂	X ₁₃	X ₁₅	X ₁₄
	10	X ₈	X ₉	X ₁₁	X ₁₀

Reset circuit = $Q_2 Q_1 + \bar{Q}_2 \bar{Q}_1 \bar{Q}_0$


We have to ensure that $reset = 1$ when 0 and 6 are present. Also the initial value of the counter is 1.

Figure 12. The reset circuit connected to the counter.

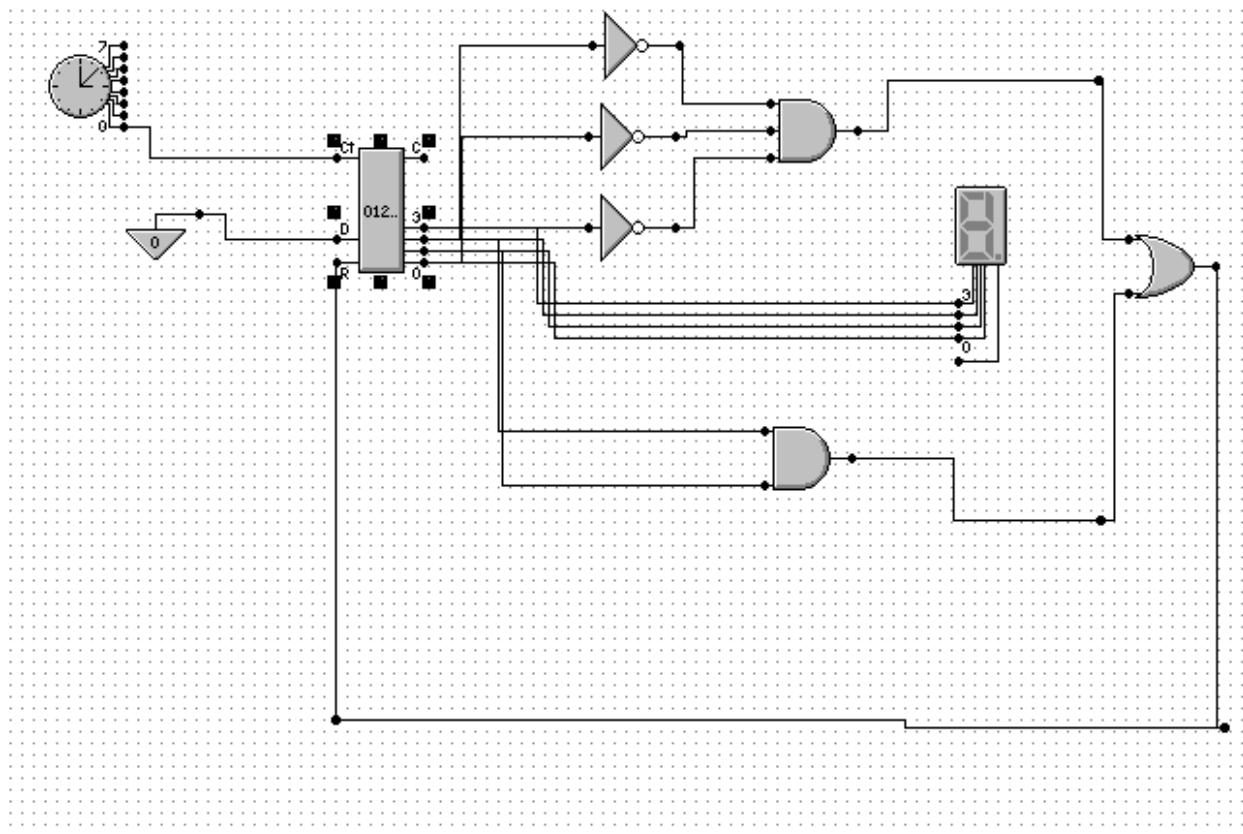

Part 3:

Figure 13. The first circuit combined with the counter.

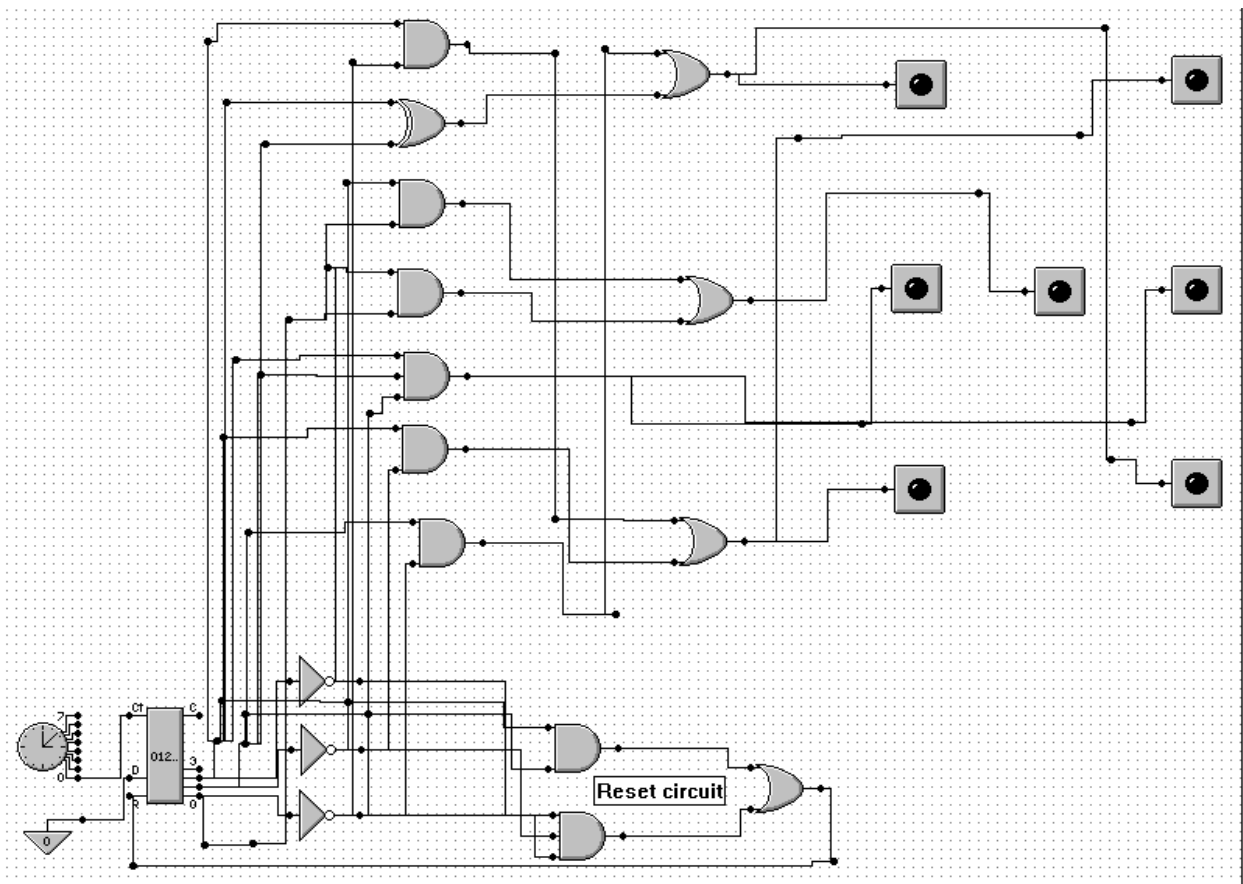

Note: The initial value of the counter is 1. It starts from 1, ends with 5, and then resets to 1. I will attach the files so you can run it by yourself.